

# **Computer Organization and Architecture**

## **In-Lab**


### **Lab 08**



Group Members Name & Reg #:	<b><u>Muhammad Haris Irfan</u></b> <b>(FA18-BCE-090)</b>
Class	Computer Organization and Architecture CPE343( <b>BCE-5B</b> )
Instructor's Name	Dr. Adeel Israr

## Inlab: Task 1

### Lab - 08 Inlab

 

```
module MealyMachine ( output reg y_out, input
    input x_in, clock, reset
);
    reg [1:0] current_state, next_state;
    parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
    always @ (current_state, x_in)
    begin
        next_state = S0;
        case (current_state)
            S0: if (x_in) next_state = S1;
            S1: if (x_in) next_state = S3;
            S2: if (x_in) next_state = S2;
            S3: if (x_in) next_state = S2;
        endcase
    end
end
```

```
always @ (posedge clock, negedge reset)
```

```
if (~reset) currentstate <= S0;
```

```
else currentstate <= next_state;
```

```
always @ (currentstate, x_in)
```

```
case (currentstate)
```

```
S0: y_out = 0;
```

```
S1, S2, S3: y_out = ~x_in;
```

```
endcase
```



Scanned with CamScanner

### Task1 Output Waveform:

